

23ECE286 CIRCUITS AND COMMUNICATION LAB

Design and implement a circuit using op-amp to generate a triangular wave with variable frequency 250 Hz to 2.5 kHz.

TERM PROJECT REPORT

Submitted by

CB.EN.U4ECE23207

Ashwin K

CB.EN.U4ECE23212

Chittesh S

CB.EN.U4ECE23227

M Rahul



AMRITA SCHOOL OF ENGINEERING

AMRITA VISHWA VIDYAPEETHAM

COIMBATORE 641112

April 2025

Date of Submission

(04/04/2025)

Students signature

Faculty

Lab Staff

Table of Contents

Topic	Page No.
Introduction	3
Objectives	3
Methodology	3
Circuit Design and Components	4
Implementation	7
Results	8
Discussion	10
Challenges and Solutions	11
Conclusion	12
References	12

Introduction

Design and implement a triangular wave generator using an op-amp (LM741) with a variable frequency range of 250 Hz to 2.5 kHz. The circuit consists of a Schmitt Trigger (comparator stage) to generate a square wave and an integrator (waveform conversion stage) to produce a triangular waveform. The design should ensure a stable and distortion-free output with smooth frequency control. The circuit is analysed through simulation to verify waveform accuracy. The project finds applications in signal processing, audio synthesis, and function generation.

Objectives

- Design a Schmitt Trigger using an LM741 op-amp to generate a square wave.
- Design an Integrator Circuit to convert the square wave into a triangular waveform.
- Select Appropriate Components (resistors and capacitors) to achieve a frequency range of 250 Hz to 2.5 kHz.
- Simulate the Circuit using LTSpice to verify waveform accuracy.
- Analyse Output Waveforms to ensure they match theoretical expectations.
- Evaluate Component Variations and their effect on frequency and amplitude.
- Implement the Circuit on Hardware using a breadboard or PCB.
- Provide a $\pm 12\text{V}$ Power Supply for proper op-amp operation.
- Test the Circuit Using an Oscilloscope to observe waveform characteristics.
- Compare Simulation and Experimental Results to validate design accuracy.

Methodology

We began by researching different triangular wave generation methods and selected a Schmitt Trigger and integrator circuit for stable waveform generation. In the design phase, we chose LM741 op-amps and calculated resistor and capacitor values to achieve a frequency range of 250 Hz to 2.5 kHz. The Schmitt Trigger used a voltage divider to set threshold voltages for square wave generation, while the integrator converted it into a triangular waveform.

- Simulated the circuit in LT Spice to verify waveform accuracy.
- Tested different resistor and capacitor values to analyze frequency variation.
- Confirmed the Schmitt Trigger's square wave and the integrator's triangular output.

After successful simulation, we assembled the circuit on a breadboard and powered it with a $\pm 12\text{V}$ supply. An oscilloscope was used to measure the output waveforms, confirming stable and adjustable triangular waves. The circuit's performance was evaluated by measuring frequency stability across different settings. Adjustments were made to optimize the design for smooth frequency control.

Circuit Design and Components

The circuit has two main stages:

1. Schmitt Trigger (Comparator Stage)

- An LM741 op-amp is used as a comparator to create the Schmitt Trigger.
- It switches between two preset voltage levels, generating a square wave.
- The output alternates between +12V and -12V as the input crosses the threshold values.

2. Integrator (Waveform Conversion Stage)

- The square wave from the Schmitt Trigger is fed into an integrator circuit.
- The integrator is built using an LM741 op-amp, a resistor, and a capacitor.
- It gradually converts the square wave into a smooth triangular waveform.

S.No	Name of The Component	Required Quantity
1.	DC Power Supply (0-200V)	1
2.	Op-Amp (LM741)	2
3.	Resistors (1kΩ, 4.7kΩ)	1 each
4.	Function Generator	1
5.	Digital Storage Oscilloscope	1
6.	Breadboard	1
7.	Connecting Wires	As Required
8.	Probes	As Required
9.	Potentiometer (4.7 KΩ- 470K Ω)	1

Component	Function
DC Power Supply (0-200V)	Provides ±15V to power the op-amp and ensures stable operation.
Op-Amp (LM741)	Used in two stages: Schmitt Trigger (generates square wave) and Integrator (converts square wave to triangular wave).
Resistors (1kΩ, 4.7kΩ)	Define Schmitt Trigger threshold voltages, control feedback for stable oscillation, and set the integration time constant in triangular wave generation.
Function Generator	Generates a 10V, 100 Hz sinusoidal input to test the Schmitt Trigger’s response to noise.
Digital Storage Oscilloscope (DSO)	Monitors output waveforms, measures switching thresholds, and verifies circuit performance.
Breadboard	Provides a platform for assembling and modifying the circuit easily.
Connecting Wires	Establishes connections between components .
Probes	Connects the oscilloscope for accurate signal measurement and analysis.

Design of Triangular Wave Generator

Let the frequency of oscillation be **1 kHz**

We have:

$$f = \frac{R_1}{4RCR_2}$$

and

$$V_{O(pp)} = 2 \frac{R_2}{R_1} V_{sat}$$

Since the supply voltage is $\pm 12V$, V_{sat} will be approximately **10V**

Let $V_{O(pp)}$ be **5V**; Assume $R_2 = 1k\Omega$.

Then,

$$R_1 = \frac{2V_{sat}}{V_{O(pp)}} R_2 = \frac{2 \times 10}{5} \times 1 \times 10^3 = 4k\Omega$$

Select the standard value,

$$R_1 = 4.7k\Omega$$

Assume **C = 0.1 μF**

$$R = \frac{R_1}{4fCR_2} = \frac{4.7 \times 10^3}{4 \times 1000 \times 0.1 \times 10^{-6} \times 1 \times 10^3} = 11.7k\Omega$$

Select the standard value,

$$R = 12k\Omega$$

To calculate the resistor R for frequencies of **250 Hz** and **2.5 kHz**, we use the given formula:

$$R = \frac{R_1}{4fCR_2}$$

Given values:

- $R_1 = 4.7k\Omega = 4700\Omega$
- $C = 0.1\mu F = 0.1 \times 10^{-6}F$
- $R_2 = 1k\Omega = 1000\Omega$

For $f = 250Hz$:

$$R = \frac{4700}{4 \times 250 \times 0.1 \times 10^{-6} \times 1000} = \frac{4700}{0.1} = 47k\Omega$$

For $f = 2.5kHz$ (2500 Hz):

$$R = \frac{4700}{4 \times 2500 \times 0.1 \times 10^{-6} \times 1000} = \frac{4700}{1}$$

$$R = 4.7k\Omega$$

So the resistor values are:

- **For 250 Hz:** $R = 47k\Omega$
- **For 2.5 kHz:** $R = 4.7k\Omega$

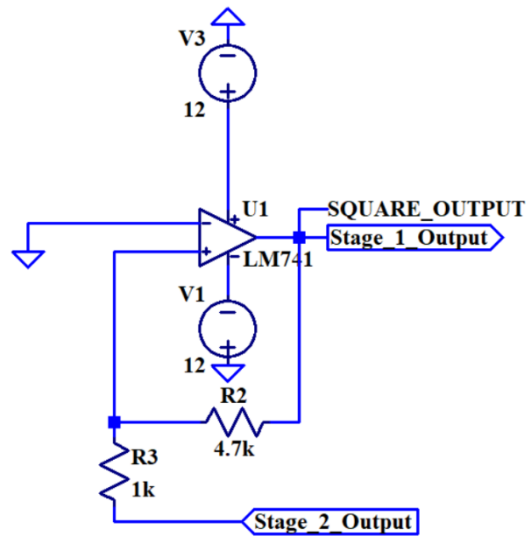


Fig. 1. Stage 1 (Schmitt Trigger)

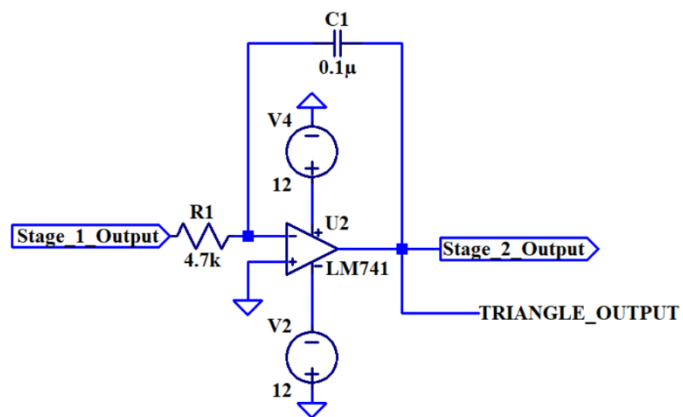


Fig. 2. Stage 2 (Integrator)

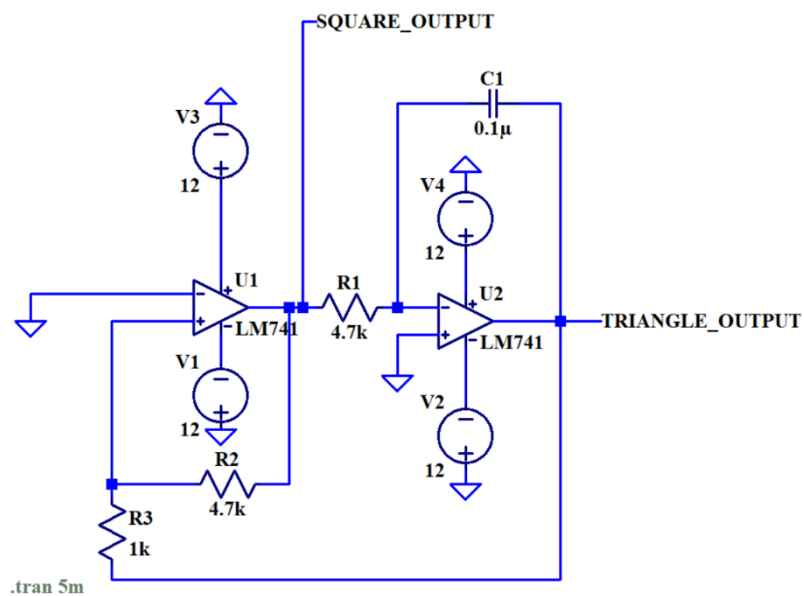


Fig. 3. Complete Circuit Diagram with both stage

Implementation

The circuit was first assembled on a breadboard, ensuring that all components were placed correctly for easy modifications. A DC power supply was set up to provide a stable $\pm 12\text{V}$ to power the LM741 operational amplifiers. Before building the full circuit, the Schmitt Trigger stage was constructed first to generate a square wave signal.

➤ **Schmitt Trigger Stage:**

- A voltage divider network was used to set the upper and lower threshold voltages.
- The input signal was applied to the inverting terminal of the op-amp through a resistor.
- Positive feedback was introduced to create hysteresis, ensuring stable square wave oscillation.

Once the Schmitt Trigger output was verified, the integrator circuit was added to convert the square wave into a triangular waveform. A capacitor and resistor network was used to perform the integration process smoothly. The circuit was then tested to confirm that the output waveform was stable and matched expectations.

➤ **Simulation and Testing:**

- The design was first simulated using LTSpice before hardware testing.
- Simulated waveforms were analysed for stability, frequency accuracy, and response to input variations.
- After confirming correct operation in the simulation, the circuit was built on hardware.

Finally, the assembled circuit was tested using a digital storage oscilloscope (DSO) to measure the output waveforms. The oscilloscope verified that the circuit generated a stable and adjustable triangular wave. The results were compared with the simulation, ensuring the design functioned correctly across the entire frequency range.

Challenges During Implementation

- **Resistor Value Mismatch:** Exact resistor values were unavailable, requiring the use of the closest standard values. This led to recalculations of threshold voltages and minor circuit adjustments to maintain proper oscillation.
- **Frequency Stability Issues:** The triangular wave frequency fluctuated slightly due to component tolerances, especially in resistors and capacitors. Using 1% tolerance components and fine-tuning resistor values improved accuracy.
- **Solution & Success:** Through careful component selection, recalibration, and iterative testing, we successfully stabilized the circuit. The final implementation produced a reliable and adjustable triangular waveform within the desired 250 Hz to 2.5 kHz range, closely matching the simulated results.

Results

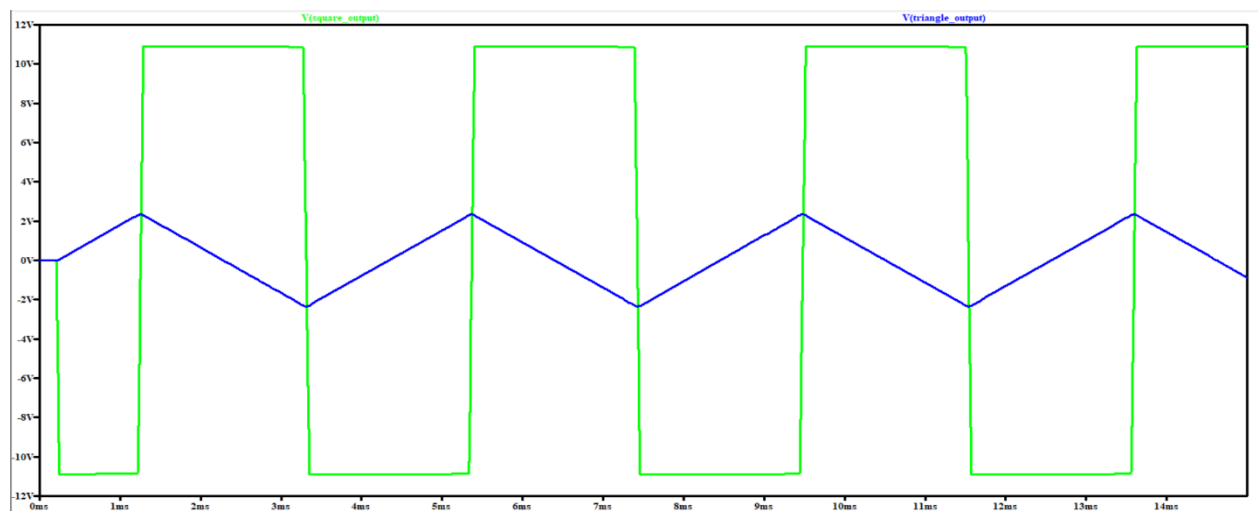


Fig. 4. Potentiometer at 47 K Ω for 250Hz

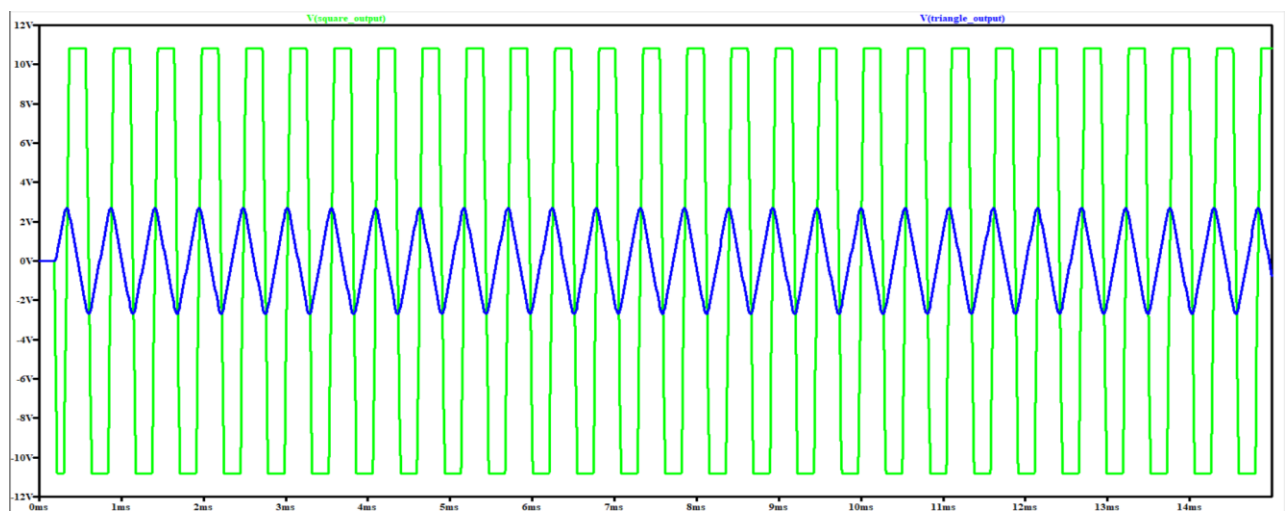


Fig. 5. Potentiometer at 4.7 K Ω for 2.5KHz

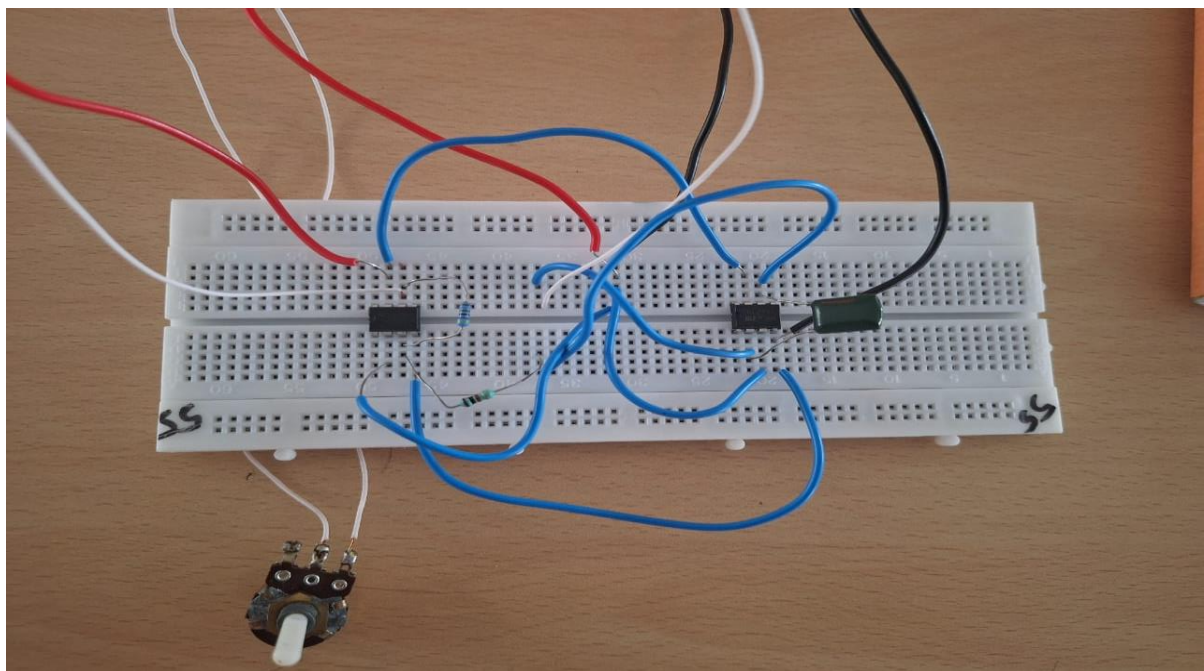


Fig. 6. Implemented Circuit in Breadboard

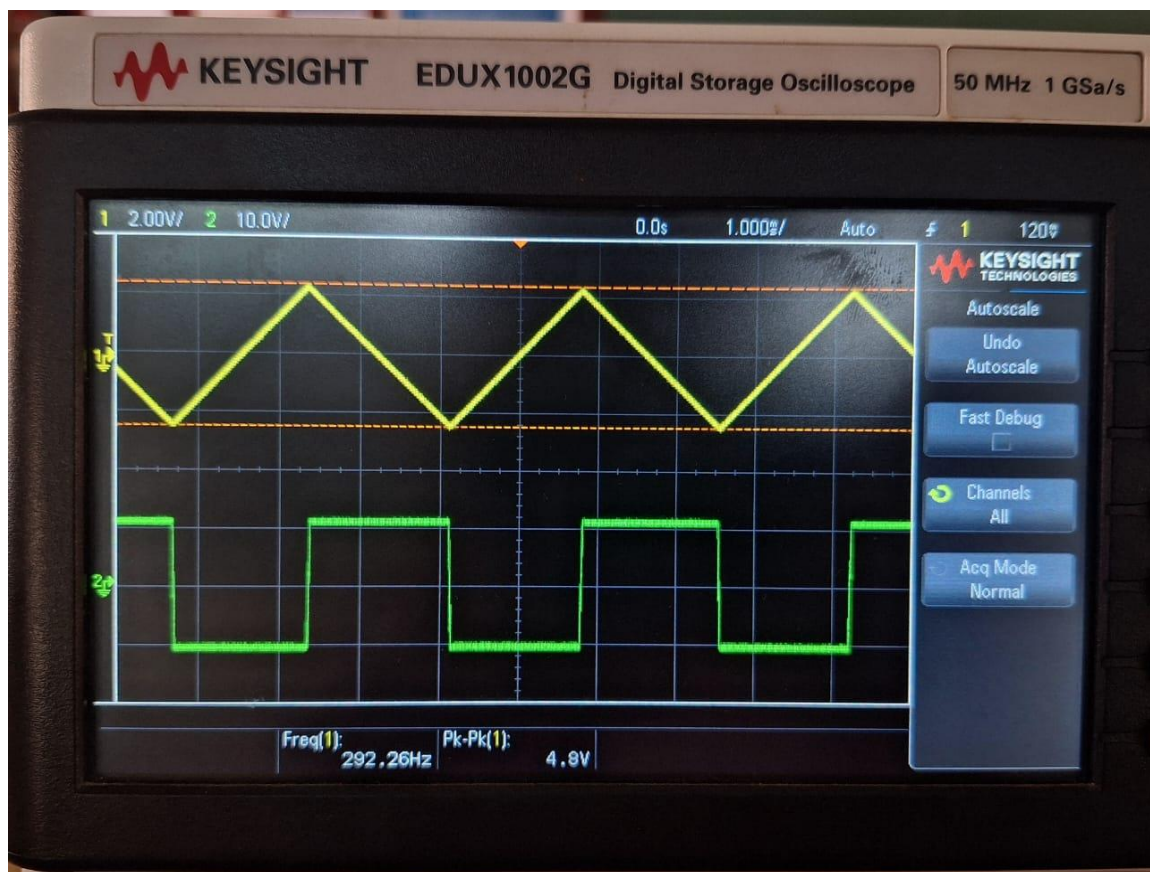


Fig. 7. Potentiometer at 47 K Ω for 250Hz (Implemented)

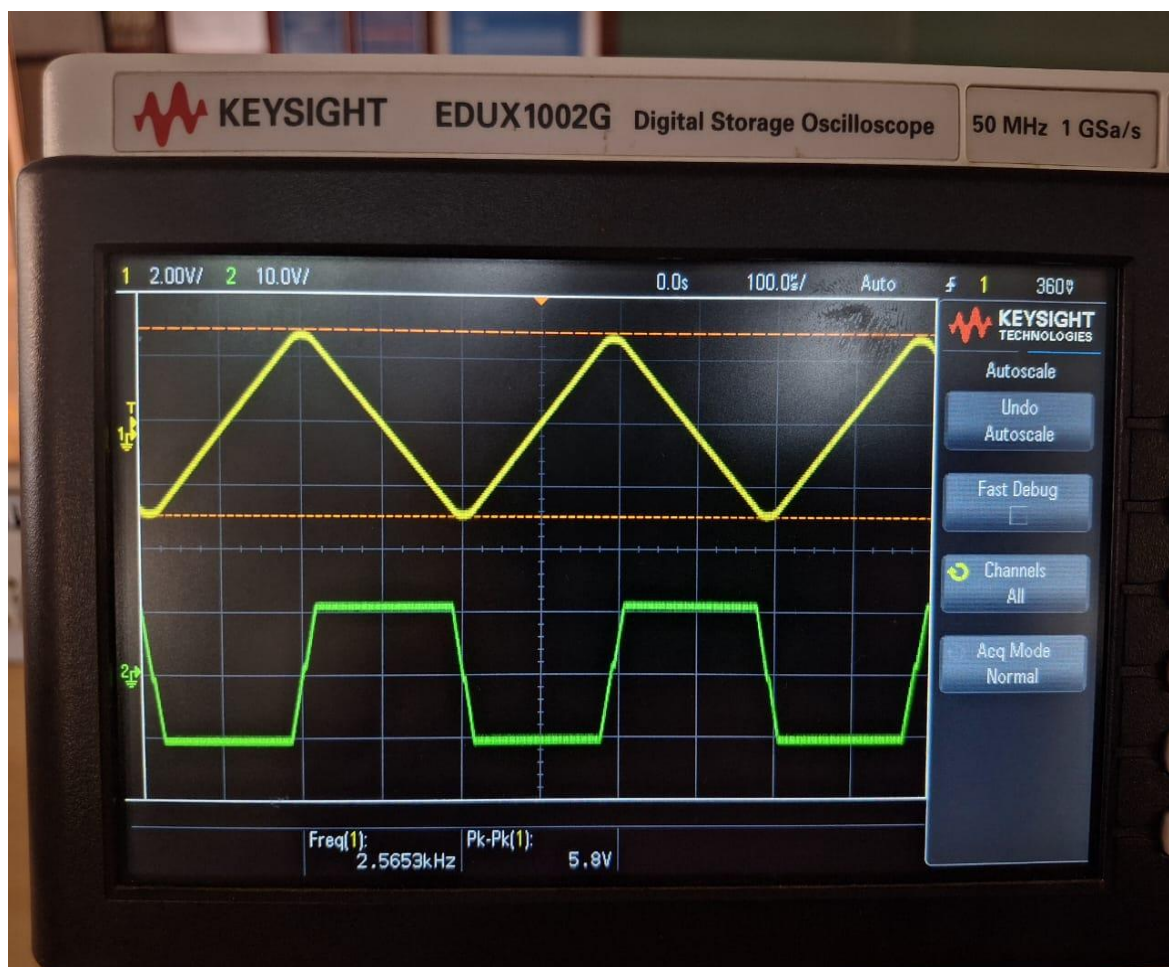


Fig. 8. Potentiometer at 4.7 K Ω for 2.5KHz (Implemented)

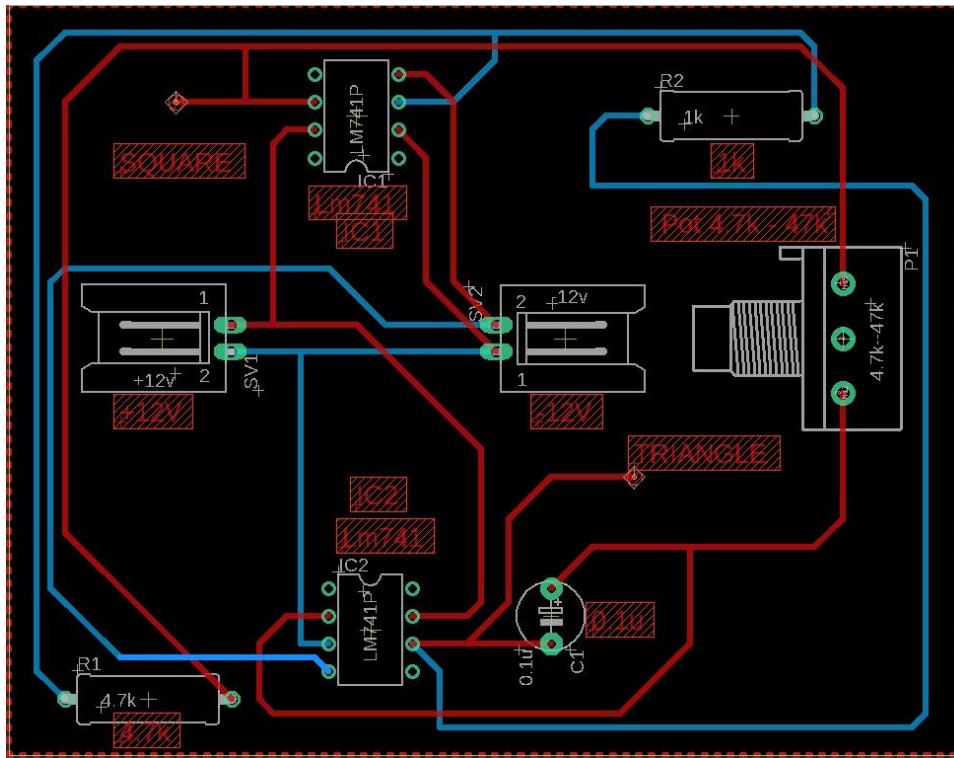


Fig. 9. PCB Layout

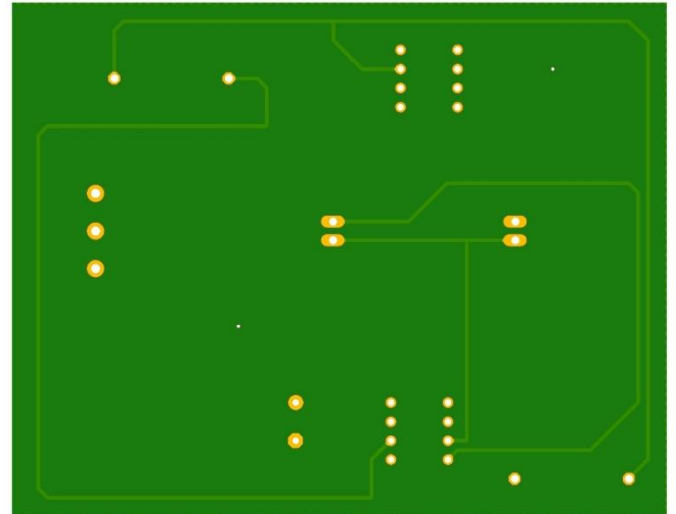
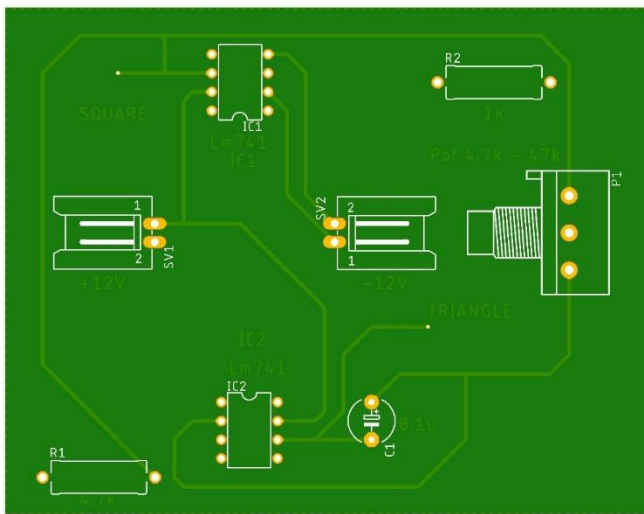


Fig. 10. Printable form PCB Front Side and Back Side

Discussion

1. Waveform Quality

- The circuit successfully generated stable and well-defined triangular waveforms, confirming its effective operation.
- Minor distortions were observed at higher frequencies due to op-amp bandwidth limitations, which could be minimized by selecting high-speed op-amps.

2. Impact of Component Selection

- The resistor and capacitor values significantly influenced the waveform's frequency, amplitude, and stability.
- Increasing the capacitor value lowered the frequency, while decreasing it resulted in a higher frequency, demonstrating the sensitivity of the circuit to passive component variations.

3. Applications of the Circuit

- Widely used in function generators for producing precise waveform signals.
- Essential in audio synthesis applications, such as musical tone generation and sound modulation.
- Plays a crucial role in signal processing circuits, including modulation systems and waveform shaping in communication systems.

Challenges and Solutions

Challenges Encountered:

Ensuring a stable triangular waveform across 250 Hz to 2.5 kHz was difficult due to component tolerances and design constraints.

1. Frequency Stability Issues – Resistor and capacitor tolerances caused variations in oscillation frequency, affecting waveform accuracy.
2. Resistor Value Mismatch – Standard resistor values didn't match calculated values, slightly altering the Schmitt Trigger's threshold.
3. Component Limitations – The LM741 op-amp had bandwidth constraints, causing minor distortions at higher frequencies.

Solutions Implemented:

To improve accuracy, we optimized component selection.

1. Precision Components – Used 1% tolerance resistors and adjusted capacitors for stable performance.
2. Threshold Adjustments – Recalculated Schmitt Trigger thresholds using available resistor values.
3. Testing & Optimization – Iterative testing with an oscilloscope helped refine resistor values and improve stability.

Conclusion

1. The circuit successfully generates a triangular wave from a square wave input.
2. The frequency of the triangular wave is adjustable within the desired range.
3. The simulation results confirm the theoretical calculations.
4. The output waveforms match expected characteristics.

This project demonstrates the design and implementation of a triangular wave generator using op-amps. The use of a Schmitt trigger and an integrator enables the generation of stable and adjustable waveforms. The circuit finds applications in function generators, signal processing, and waveform synthesis.

References

- [1] Sedra A and Smith K C, *Microelectronic circuits*, 6th ed. New York: Oxford University Press, 2010.
- [2] Texas Instruments, "Designing With Operational Amplifiers: Basics and Best Practices," *Texas Instruments Application Report*, Apr. 2013. [Online]. Available: <https://www.ti.com/lit/pdf/tidu020>